

Date of experiment – 15/2/2024

Date of report – 24/2/2024

Lab Report 3

AC Circuits

Experiment conducted by: Gurraunak Singh Bedi

Lab Partner: Thomas Cesare Bolton

Abstract

This experiment was conducted in order to comprehend the oscilloscope's Sinusoidal plots. Understanding the phase shift between the voltage and the current was the secondary goal. This was done by measuring the peak-to-peak AC voltage and deriving the current and phase-shift in three different kinds of circuits for different values of AC frequency. These circuits were RC, RL and only Resistance circuits respectively. The current (I) flowing in the RC circuit was $0.52 \pm 0.03 \text{mA}$ and the phase-shift showed an exponential and then a gradual increase with decrease in reactance. On the other hand, the current (I) flowing in the RL circuit was $0.803 \pm 0.013 \text{mA}$ and the phase-shift showed a decrease with increase in reactance. For the resistance only circuits there was no phase-shift as there was no reactance.

Introduction

The key concepts involved in this experiment were Sinusoidal motion, AC voltage (peak to peak), Capacitance, Inductance, Reactance, Phase-shift, Oscilloscope (Vertical Gain, Horizontal time base)

A periodic wave with the waveform or shape of the trigonometric sine function is called a sine wave, sinusoidal wave, or sinusoid. A characteristic that makes periodic waves different is that any two sine waves with the same frequency (but arbitrary phase) can be joined linearly to produce another sine wave with the same frequency. On the other hand, a sine wave of any phase can be expressed as the linear combination of two sine waves, the sine and cosine components, having phases of zero and a quarter cycle, respectively, if a certain phase is selected as the zero reference. The general form of a sine wave of any arbitrary phase is given by -:

$$y(t) = A \sin(\omega t + \varphi) \quad (1)$$

Where t represents time, ω represents angular frequency, A represents amplitude and φ is the phase shift

This principle is observed in AC circuits as well. The magnitude of the current and voltage vary sinusoidally. The phase shift depends on the type of circuit used. In a RC circuit, the voltage leads the current by an angle of -:

$$\varphi = \tan^{-1} \left(\frac{X_c}{R} \right) \quad (2)$$

Where X_c is the Reactance Capacitance and R is the external resistance. X_c is the resistance offered to the flow of AC current through the capacitor. This is given by -:

$$X_c = \frac{1}{2\pi\nu C} \quad (3)$$

Where ν is the frequency and C is the capacitance of the capacitor. Capacitance is the capability of a material object or device to store electric charge. It is measured by the charge in response to a difference in electric potential, expressed as the ratio of those quantities.

In a RL circuit, the current leads the voltage by an angle of -:

$$\varphi = \tan^{-1} \left(\frac{X_l}{R} \right) \quad (4)$$

Where X_l is the Reactance Inductance and R is the external resistance. X_l is the resistance offered to the flow of AC current through the Inductor. This is given by -:

$$X_l = 2\pi\nu L \quad (5)$$

Where ν is the frequency and L is the inductance of the inductor. Inductance is the tendency of an electrical conductor to oppose a change in the electric current flowing through it. It is defined as the ratio of the induced voltage to the rate of change of current causing it. It is a proportionality constant that depends on the geometry of circuit conductors and the magnetic permeability of the conductor and nearby materials

The key instrument used in this experiment, to measure the AC voltage (peak-to-peak), was the oscilloscope. An oscilloscope is a kind of electrical test device that shows the voltage variations of one or more signals graphically over time. After the waveform is shown, many characteristics can be examined, including distortion, amplitude, frequency, rise time, and time interval. For this experiment the vertical gain (voltage base) was measured for the voltage and the horizontal time base was manipulated to measure the frequency.

The other principles used in the calculation for this experiment were uncertainties and errors. There were three types of errors involved –

Instrumental error – Errors that occur due to the minimum scaling of the non-digital instrument where, it may be possible to estimate additional figures. Hence, the instrumental error can be taken as \pm half of the smallest unit.

Systematic error – Common mistakes constant throughout the entire experiment, such as incorrect calibration of instrument or human error such as reaction time, etc.

Random error – Small and unpredicted fluctuations in either the technique or the environment that alter the results of the experiment.

To express the error of data sets, two methods were used, described in detail in subsequent pages of this report -

Statistical analysis of large data sets

Linest function in excel

The final principle used was error propagation. The error of the quantities, which were combined in a formula to get the result, gave rise to new errors. Therefore, to work out these new errors, the formulas, listed below, were used –

Addition and Subtraction	$z = x \pm y$	$\Delta z = \sqrt{(\Delta x)^2 + (\Delta y)^2}$	(6)
--------------------------	---------------	---	-----

Multiplication and Division	$z = xy \text{ or } \frac{x}{y}$	$\Delta z = z \sqrt{\left(\frac{\Delta x}{x}\right)^2 + \left(\frac{\Delta y}{y}\right)^2}$	(7)
-----------------------------	----------------------------------	---	-----

Powers	$z = x^n$	$\Delta z = n x^{n-1} \Delta x$	(8)
--------	-----------	-----------------------------------	-----

Constant	$z = Cx$	$\Delta z = C \Delta x$	(9)
----------	----------	---------------------------	-----

To minimize the error on the readings, repeated readings were taken. This minimized the systematic and random errors

Method

Calibration of Frequency

For the first step, the frequency dial of the AC generator needed to be calibrated. The diagram given below was followed to setup the AC function generator to produce a sinusoidal wave of frequency 100 Hz -:

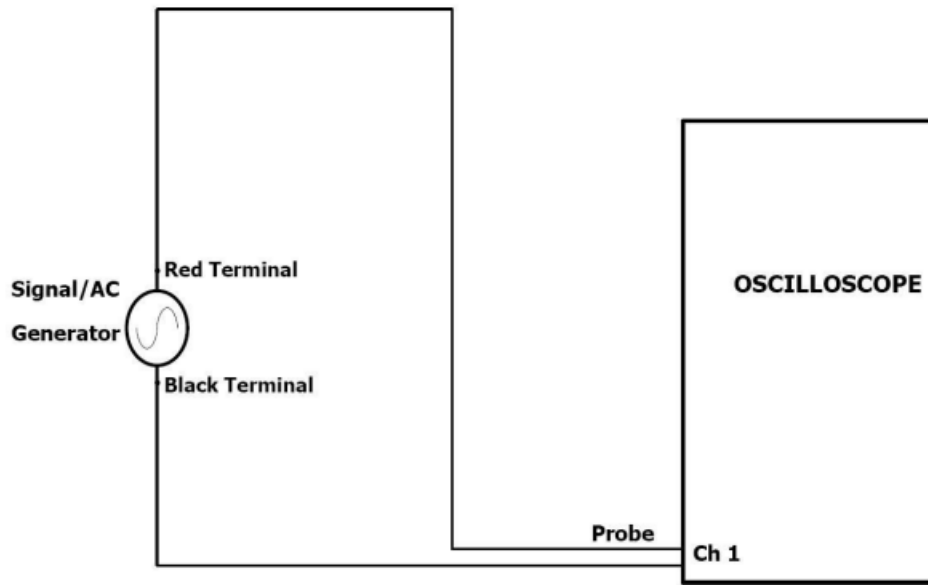


Figure 1 circuit for calibrating the frequency

The output voltage was set to 5V. The time division dial was set to 10ms and the vertical gain was adjusted till the amplitude of the wave fill the screen. Repeated readings were taken for a range of frequencies between 100 Hz and 5000 Hz

The RC circuit

The circuit, for this part of the experiment, was setup according to the diagram given below -:

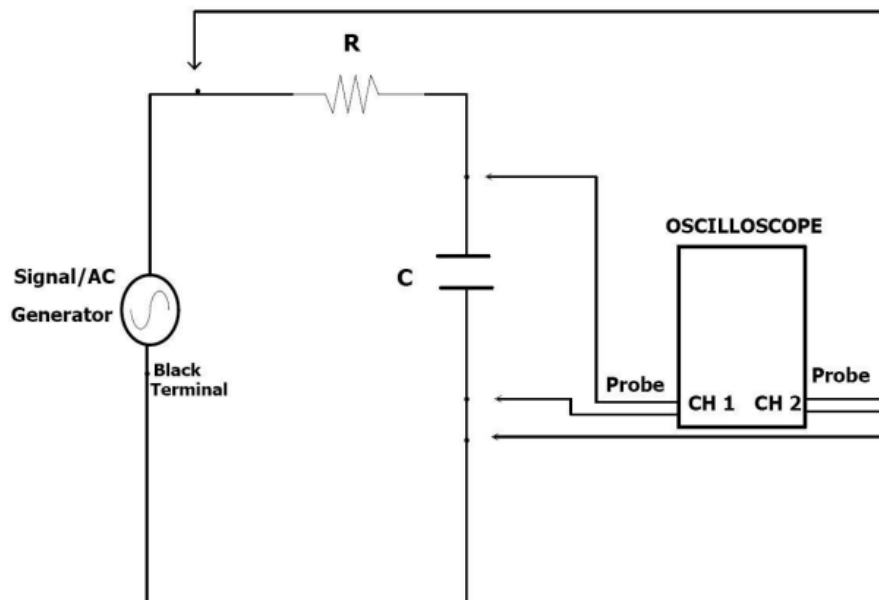


Figure 2 RC circuit

The value of the capacitor was set to be $0.2\mu\text{F}$ and the resistor used was a $5\text{k}\Omega$ resistor. The peak-to-peak voltage was set, similar to the earlier part, as 5V. The voltage across ch1 (V_c) was measured by the oscilloscope. Repeated readings were taken for a range of frequencies between 100 Hz and 5000 Hz. Also, the phase difference between the voltage across reactance and the impedance was measured

The RL circuit

A similar set up, as the previous part, was used in this part of the experiment except, the capacitor was replaced by an inductor of inductance of 100mH. Otherwise, the circuit and the value of all the components remained same.

Similar as before, repeated readings were taken for a range of frequencies between 100 Hz and 5000 Hz and the phase difference was measured

Resistors in series

Same as before, the inductor was replaced by a resistor of 5k Ω . Now the circuit became a resistance-based series circuit.

For this part, only three readings were taken for 100Hz, 1000Hz and 5000Hz respectively.

Results

Calibration of the frequency

The results for this part of the experiment are as follows -:

calculated f	Given f
100	100
500	500
1000	1000
1515	1500
2000	2000
2500	2500
3030	3000
3472	3500
4032	4000
4545	4500
5000	5000

Table 1 calculated frequency

The calibration error for the oscilloscope was estimated to be 0.002%, which was negligible. Therefore, it was ignored and the AC generator and the oscilloscope were correctly calibrated.

The RC Circuit

The measured V_c and the calculated X_c , using formula (3), are given as follows -:

frequency	voltage	reactance
100.000	4.240	7957.747
500.000	1.600	1591.549
1000.000	0.840	795.775
1500.000	0.580	530.516
2000.000	0.420	397.887
2500.000	0.340	318.310
3000.000	0.290	265.258
3500.000	0.240	227.364
4000.000	0.220	198.944
4500.000	0.190	176.839
5000.000	0.180	159.155

Table 2 results for RC circuit

The error for the above calculation was calculated using formulas (8) and (9). They are given as follows -:

ΔV	frequency	voltage	reactance	Δf	ΔR_c
0.005	100.000	4.240	7957.747	0.001	0.200
0.005	500.000	1.600	1591.549	0.001	1.000
0.005	1000.000	0.840	795.775	0.001	2.000
0.005	1500.000	0.580	530.516	0.001	3.000
0.005	2000.000	0.420	397.887	0.001	4.000
0.005	2500.000	0.340	318.310	0.001	5.000
0.005	3000.000	0.290	265.258	0.001	6.000
0.005	3500.000	0.240	227.364	0.001	7.000
0.005	4000.000	0.220	198.944	0.001	8.000
0.005	4500.000	0.190	176.839	0.001	9.000
0.005	5000.000	0.180	159.155	0.001	10.000

Table 3 results with uncertainties

Two graphs were formulated out of the above given data. One was for Voltage vs Reactance capacitance which is given below -:

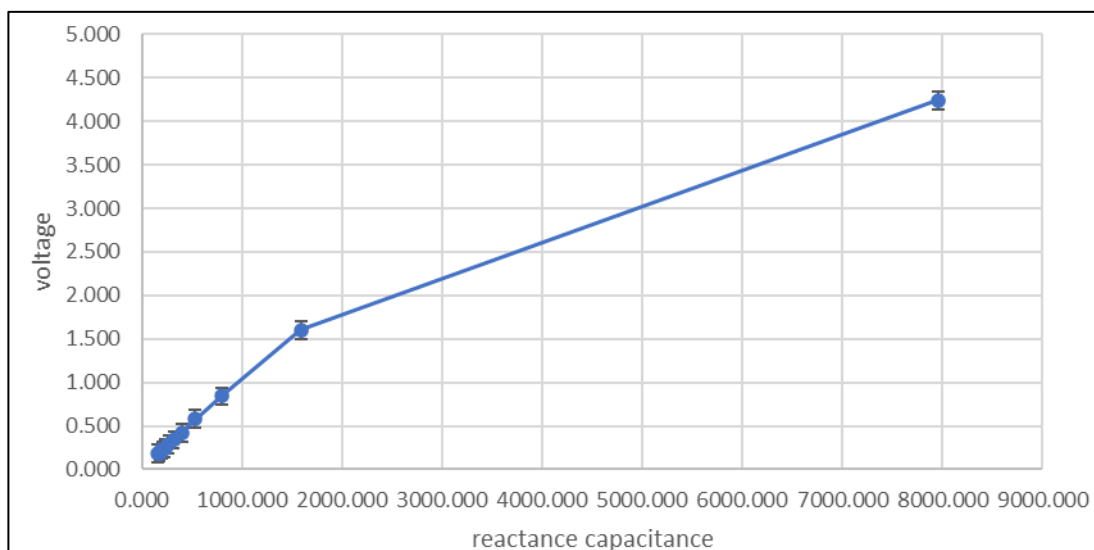


Figure 3 graph of voltage vs reactance

Form the graph, it was worked out that $V_c \propto X_c$ and the gradient for this graph represented the current (I) flowing through the circuit. This was derived using the formula -:

$$V_c = \frac{I}{2\pi fC} = IX_c \quad (10)$$

The value of the gradient I derived using the LINEST function was found out to be $0.52 \pm 0.03 \text{mA}$

The other graph made was for voltage vs frequency. This is given below -:

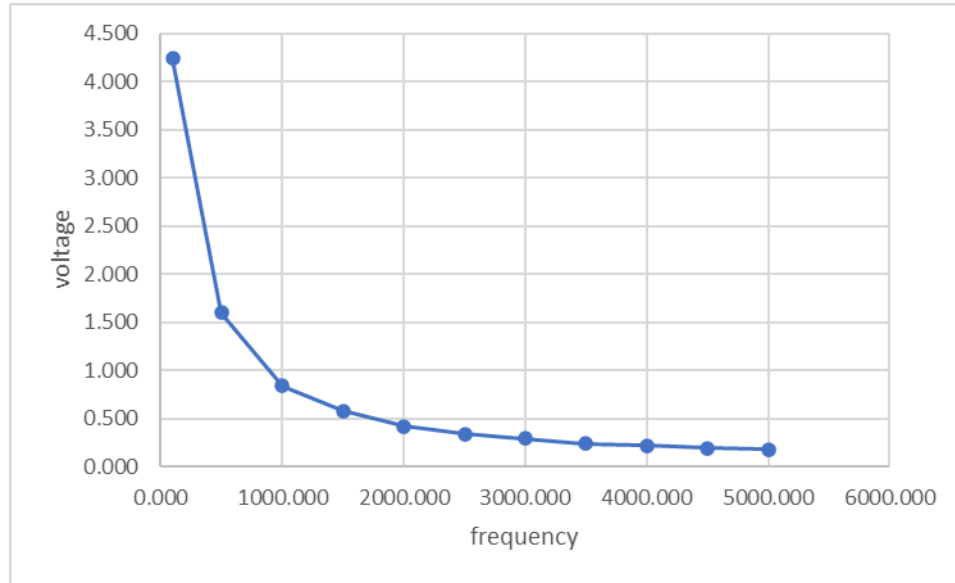


Figure 4 graph of voltage vs frequency

This graph showed that as frequency increases, voltage decreases. Therefore, the gradient was found out to be negative

$\therefore V_c \propto \frac{1}{f}$

The phase for the capacitor only is I leads V by $\frac{\pi}{2}$. Phase for the reactance derived by formula (2) is given below -;

frequency	reactance	impedance phase	phase shift
100.000	7957.747	57.858	32.142
500.000	1591.549	17.657	72.343
1000.000	795.775	9.043	80.957
1500.000	530.516	6.057	83.943
2000.000	397.887	4.550	85.450
2500.000	318.310	3.643	86.357
3000.000	265.258	3.037	86.963
3500.000	227.364	2.604	87.396
4000.000	198.944	2.279	87.721
4500.000	176.839	2.026	87.974
5000.000	159.155	1.823	88.177

Table 2 phase shift for RC circuit

A shot taken for the observed phase shift for 100Hz is given below -:

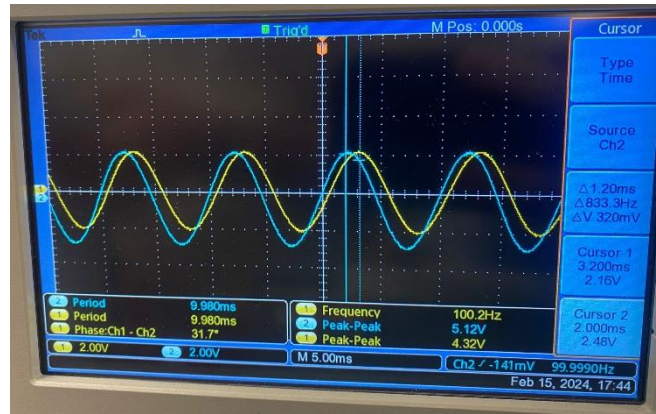


Figure 5 graph for phase shift of RC circuit

The RL Circuit

Similar to the previous part, the measured V_L and the calculated X_L , using formula (5), are given as follows -:

frequency	voltage	reactance
100.000	0.220	62.832
500.000	0.360	314.159
1000.000	0.620	628.319
1500.000	0.900	942.478
2000.000	1.220	1256.637
2500.000	1.460	1570.796
3000.000	1.720	1884.956
3500.000	1.960	2199.115
4000.000	2.200	2513.274
4500.000	2.400	2827.433
5000.000	2.620	3141.593

Table 5 results for RL circuit

The error for the above calculation was calculated using formulas (8) and (9). They are given as follows -:

frequency	voltage	reactance	delta f	delta R_L
100.000	0.220	62.832	0.001	0.079
500.000	0.360	314.159	0.001	0.395
1000.000	0.620	628.319	0.001	0.790
1500.000	0.900	942.478	0.001	1.184
2000.000	1.220	1256.637	0.001	1.579
2500.000	1.460	1570.796	0.001	1.974
3000.000	1.720	1884.956	0.001	2.369
3500.000	1.960	2199.115	0.001	2.763
4000.000	2.200	2513.274	0.001	3.158
4500.000	2.400	2827.433	0.001	3.553
5000.000	2.620	3141.593	0.001	3.948

Table 6 results with uncertainties

Two graphs were formulated out of the above given data. One was for Voltage vs Reactance inductance which is given below -:

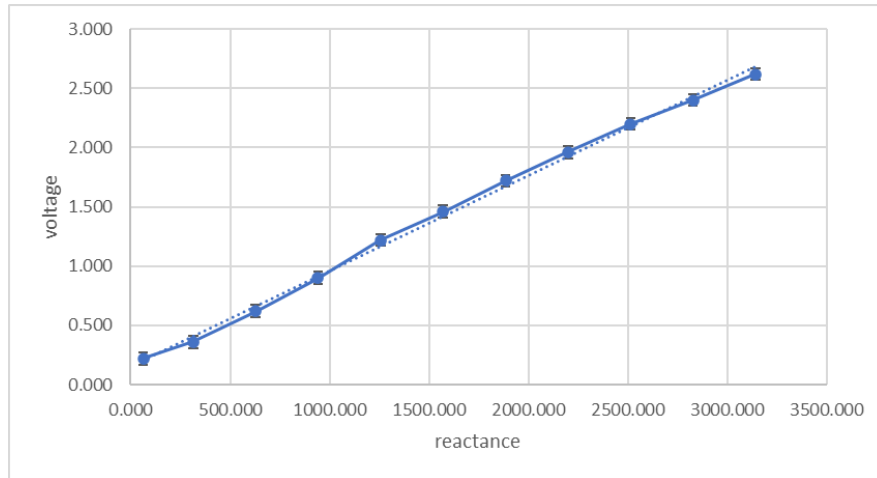


Figure 6 graph of voltage vs reactance

Form the graph, it was worked out that $V_l \propto X_l$ and the gradient for this graph represented the current (I) flowing through the circuit. This was derived using the formula -:

$$V_c = I2\pi fL = IX_l \quad (11)$$

The value of the gradient I derived using the LINEST function was found out to be $0.803 \pm 0.013 \text{mA}$

The other graph made was for voltage vs frequency. This is given below -:

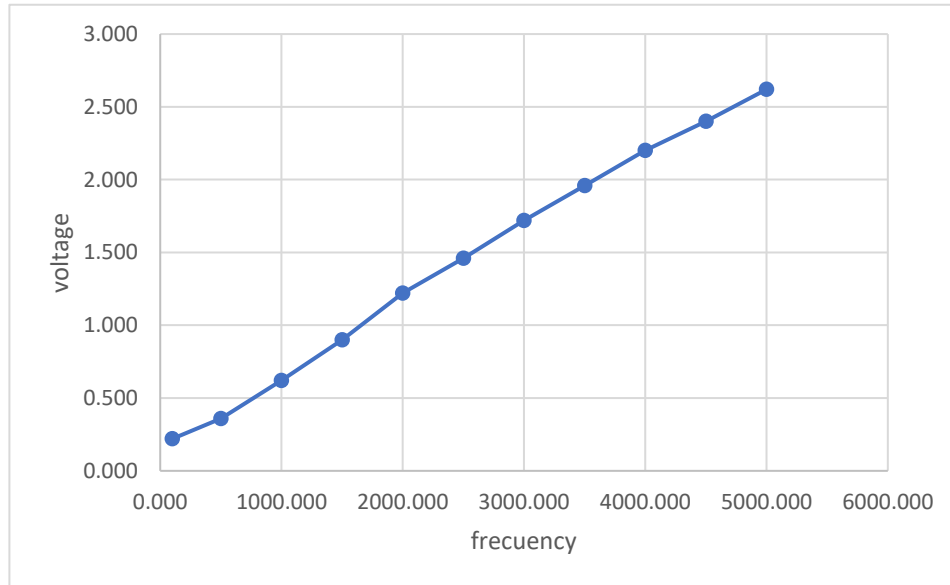


Figure 6 graph of voltage vs frequency

This graph showed that as frequency increases, voltage increases. Therefore, the gradient was found out to be positive

\therefore

$$V_l \propto f$$

The phase for the inductors only is V leads I by $\frac{\pi}{2}$. Phase for the reactance derived by formula (4) is given below -;

frequency	reactance	impedance phase	phase shift
100.000	62.832	0.720	-89.280
500.000	314.159	3.595	-86.405
1000.000	628.319	7.162	-82.838
1500.000	942.478	10.675	-79.325
2000.000	1256.637	14.108	-75.892
2500.000	1570.796	17.441	-72.559
3000.000	1884.956	20.656	-69.344
3500.000	2199.115	23.741	-66.259
4000.000	2513.274	26.687	-63.313
4500.000	2827.433	29.488	-60.512
5000.000	3141.593	32.142	-57.858

Table 7 phase shift for RL circuit

A shot taken for the observed phase shift for 1500Hz is given below -:

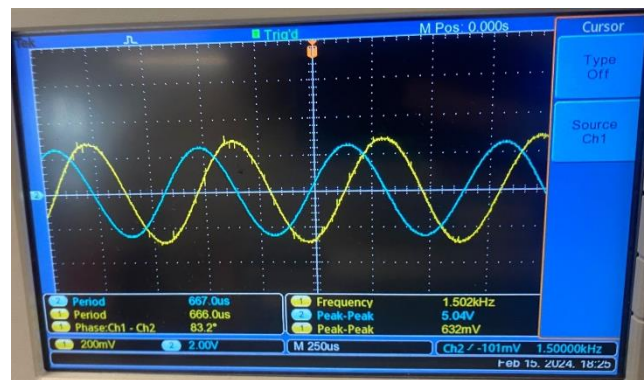


Figure 8 graph for phase shift of RL circuit

Resistors in series

For this part, only three readings were taken for frequencies 100Hz, 1000Hz and 5000Hz. For all three frequencies the V was 2.5V and the total resistance was 10000Ω. There was also, no phase-shift as there was no reactance in play.

Discussion

For the first part of the experiment, the calibration of the frequency had negligible error of 0.001% deviation from the input value. This error could be due to the heating up of equipment during the process. This error was classified as a systematic error that was minimized by taking multiple readings.

For RC and RL circuits both, the voltage showed an increase with increase in reactance, displaying that V is directly proportional to reactance. However, RC circuits showed an exponential growth, while RL circuits displayed a more linear growth. While systematic error like heating up of equipment, the parallax of the eye while adjusting the horizontal and vertical knobs and other errors, were present, the errors of the oscilloscope were also taken into consideration. These errors were minimized by taking multiple readings for different values of frequency.

In RC circuits, the voltage vs frequency graph showed that $V_c \propto \frac{1}{f}$, but on the other hand the same graph in RL circuit, displayed that $V_l \propto f$. However, in the resistance only circuit the reactance is zero, therefore, for every frequency the voltage remains the same.

For the phase-shift, both the circuits showed that ϕ is directly proportional to the reactance in the circuit. The resistance only circuit did not display any phase-shift as there is no reactance present in the circuit.

Conclusion

The purpose of this experiment was to understand the Sinusoidal graphs on the oscilloscope. The secondary objective was to comprehend the phase shift that occurs between the voltage and the current. In order to do this, the peak-to-peak AC voltage in three distinct circuit types was measured, and the current and phase-shift were calculated for various AC frequency values. These circuits were merely resistance, RL, and RC circuits, in that order. The RC circuit's current flowed at 0.52 ± 0.03 mA, and the phase-shift revealed an exponential increase at first, followed by a steady increase as the reactance decreased. In contrast, the RL circuit's current (I) was 0.803 ± 0.013 mA, and as reactance increased, the phase-shift decreased. Since there was no reactance in the resistance-only circuits, there was no phase shift.

References

Young, Hugh, and Roger Freedman. University Physics with Modern Physics, Global Edition, Pearson Education, Limited, 2019.

Hughes, Ifan, and Thomas Hase. Measurements and Their Uncertainties: & Practical Guide to Modern Error Analysis, Oxford University Press, Incorporated, 2010.

<https://en.wikipedia.org/wiki/Oscilloscope> accessed 23/02/24

https://en.wikipedia.org/wiki/Sine_wave accessed 23/02/24